

### Previous Knowledge

Some things are plugged in and some things need batteries to make them work

### Project Hook or 'Wow' memory

Create a light up nose on a clown face

### The key skills we want pupils to use during this topic:

Ask relevant **questions** and use different types of scientific enquiries to answer them. Set up simple practical investigations, **compare** things and make **fair tests**. Make careful **observations** and take **accurate measurements** using the right units using a range of equipment.

Gather, record, sort and **present data** in a variety of ways to help in **answering questions**. Record findings using simple **scientific language**, drawings, labelled diagrams, keys, bar charts and tables.

Report findings by talking and writing about them, displaying or **presenting results** and **conclusions**. Use results to draw simple conclusions, make **predictions**, suggest **improvements** and ask more questions. **Identify differences, similarities or changes**. Use clear **scientific evidence** to answer questions or to support my findings.

#### Learning Steps

#### Key Knowledge (answers)

How would you group these electrical devices based on where the electricity comes from? **(Identifying classifying)**


Elicitation activity—mind map  
Lightning and static electricity occur naturally  
Mains electricity is created  
Batteries are stored electricity

Which room has the most electrical sockets in your house? **(Pattern spotting)**

Kitchen has the most  
Bathrooms have the least  
Use collected data to reason why and analyse

How does a light bulb work? **(Research)**

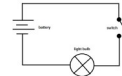A circuit is made when a complete loop is created with a battery and the bulb lights up.  
Create a circuit and label the parts.



How long does a battery last in a torch? **(Observing over time)**

Different batteries last longer than others.

Which circuits will make the lamp light? **(identifying and classifying)**

A circuit is complete and will make the bulb light when all the parts are connected correctly.

Which materials are conductors / insulators of electricity? **(Identifying and classifying)**

Metals are good materials to use as electrical conductors  
Not all materials are good conductors of electricity

Which metal is the best conductor of electricity? **(Comparative testing)**

How does a switch work? **(C)**

A switch turns an electrical current off and on

### Key vocabulary

<b>Electricity</b>	The flow of an electric current or charge through a material
<b>Generate</b>	To make or produce
<b>Renewable</b>	Source of electricity that will not run out—solar, nuclear, geothermal, wind, hydro
<b>Non-renewable</b>	Source of electricity that will run out—fossil fuels: coal, natural gas, oil
<b>Appliances</b>	A piece of equipment or device designed to perform a particular job—TV, dryer
<b>Battery / cell</b>	A device that stores electrical energy
<b>Circuit</b>	A pathway that electricity can flow around—wires, power supply, bulbs, switches
<b>Electrons</b>	Small particles with an electric charge

#### Statutory Requirements

Identify common appliances that run on electricity  
Make a simple electrical circuit, identifying and naming its basic parts: cells, wires, bulbs, switches and buzzers.  
Identify whether or not a lamp will light in a simple circuit, based on whether or not the lamp is part of a complete loop with a battery.  
Recognise some common conductors and insulators, and associate with metals being good conductors

